

SOUTHERN ILLINOIS UNIVERSITY  
DEPARTMENT OF ELECTRICAL AND COMPUTER  
ENGINEERING

---

# ASIC Design Final Project

---

Implementation of ANN to predict Handwritten Digits

*Submitted By:*

Shraddha Dahal (856489270)

Aashish Itani (856300090)

December 4, 2020

In this project, we implement a 3 layer artificial neural network to recognize the hand-written digits correctly. The input are 8\*8 pixel images with each pixel ranging from -0.5 to 0.5. These values are represented by 8-bit fixed point 2's complementary numbers with 7 fractional bits.

### 1. MAC

The first part of the project involved in design of MAC(Multiplier and Accumulator Circuit). The block diagram of MAC circuit is presented in figure 1. The module

 


Figure 1: MAC block diagram

computes

$$y = \sum_{i=1}^{16} w_i \cdot x_i \quad (1)$$

where  $w_i$  and  $x_i$  are 8-bit fixed point numbers.

The schematic of designed MAC module is in figure 2. We have used pipeline register and on running the synthesis using timing constraint with clock period 10 ns, the Worst Negative slack is 12.601 ns for the hold time satisfies with Worst Hold Slack of 0.511 ns.

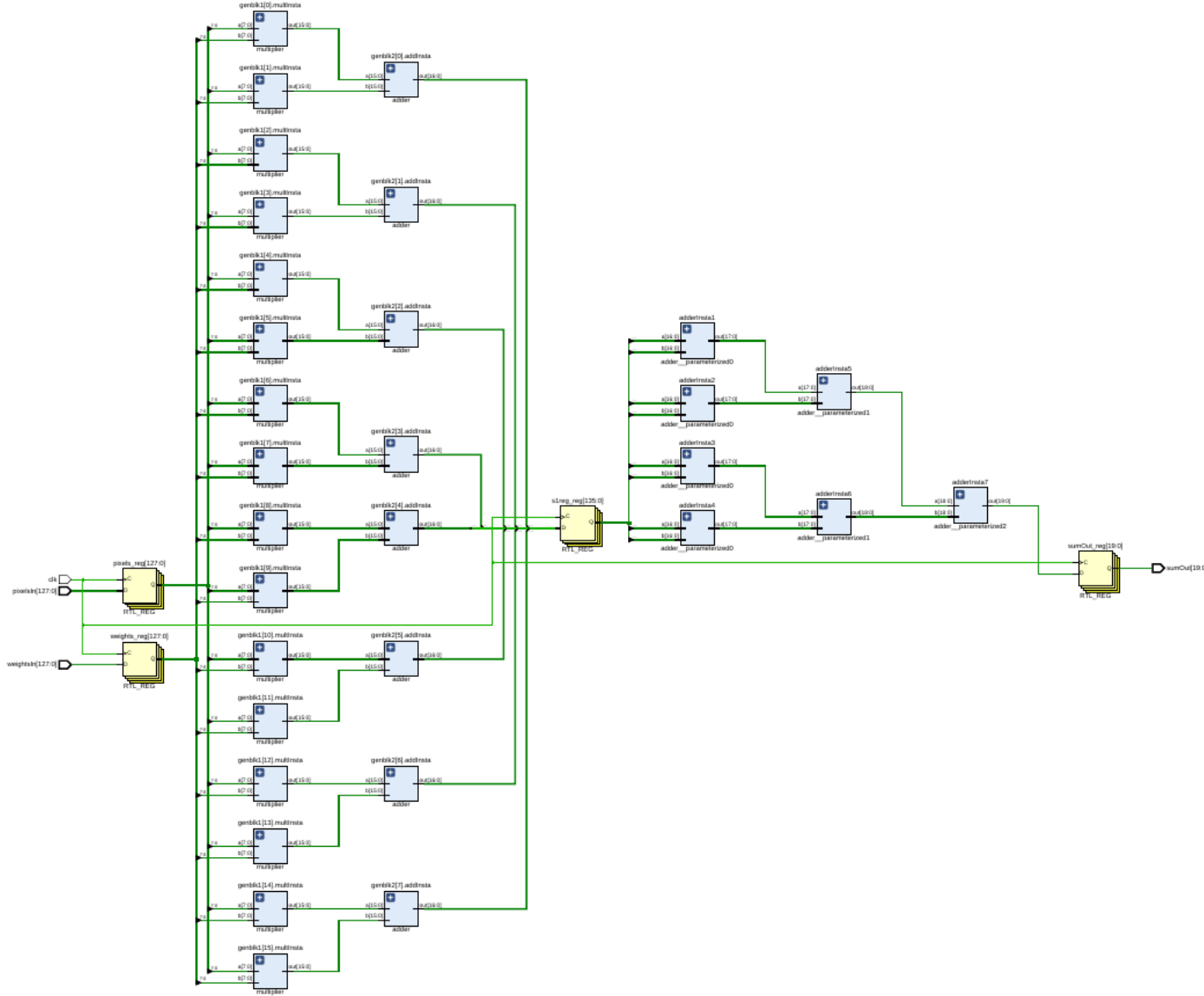


Figure 2: MAC block diagram

#### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 12.601 ns	Worst Hold Slack (WHS): 0.511 ns	Worst Pulse Width Slack (WPWS): 9.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 156	Total Number of Endpoints: 156	Total Number of Endpoints: 413

All user specified timing constraints are met.

Figure 3: Timing Summary

## 2. ACC

The MAC module does computation for 16 multiplications and adds them together. Since we need to add 64 multiplications to get output of the hidden node, we need to use MAC module for 4 clock cycles. In first clock cycle, we add the bias. The

weighted sum performed by ACC module is

$$y = \sum_{i=1}^N w_i \cdot x_i + b_i \quad (2)$$

After that, we add for 3 clock cycles. The Accumulator schematic is shown in figure 4. An FSM is designed to control the accumulator and a MUX is used to either select bias or the previous accumulator value to be added to the input.

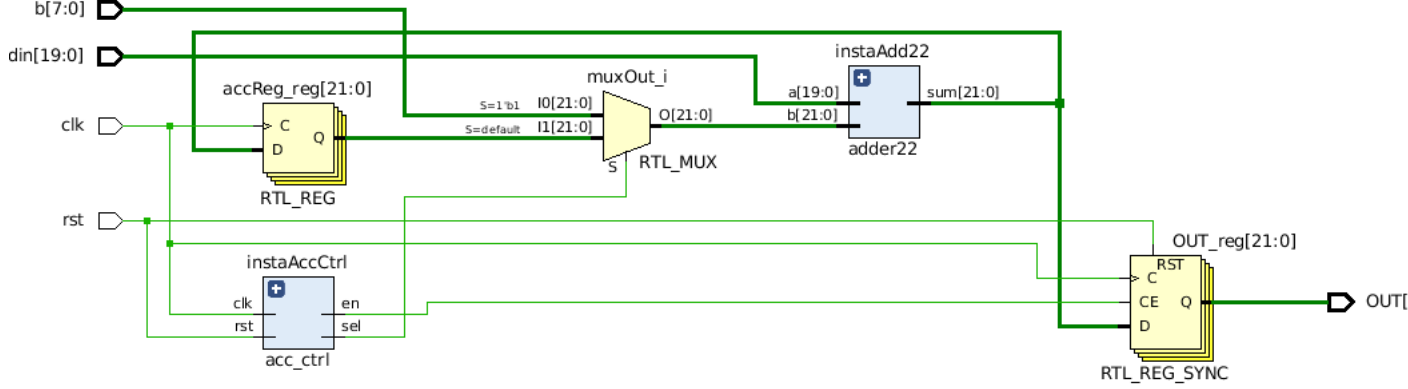


Figure 4: ACC Schematic

### 3. MAC\_ACC

We now connect the MAC and ACC modules together to form a MAC\_ACC module. The schematic of MAC\_ACC module is in figure 5.

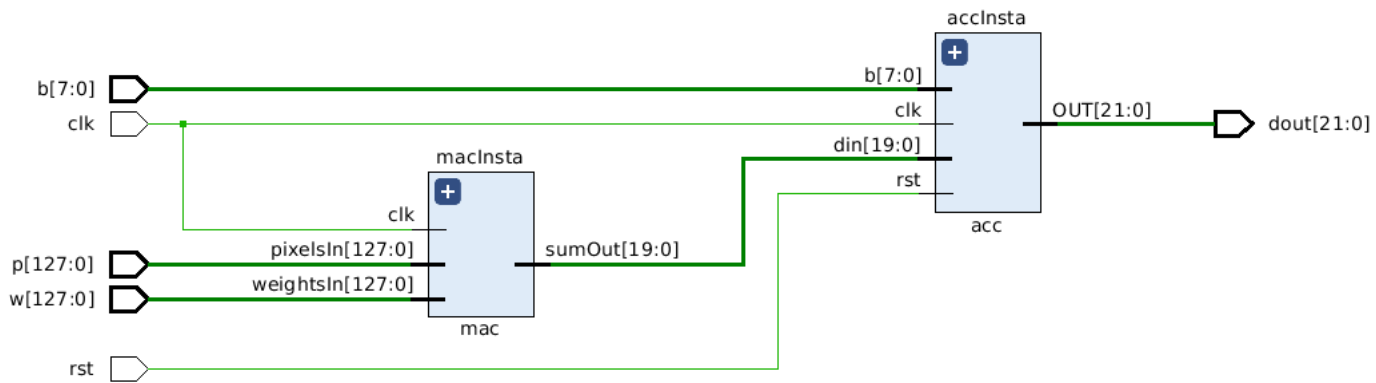


Figure 5: MAC\_ACC Schematic

### 4. Sigmoid\_func

We created a sigmoid\_func module. The sigmoid\_func module consists of sig-

moid\_IP and the IP wrapper. The sigmoid IP is an activation function that computes

$$f(y) = \frac{1}{1 + e^{-y}} - 0.5 \quad (3)$$

The IP wrapper module takes the 22 bit output of MAC\_ACC module and generates signals ovf and sign. These signals are fed to the sigmoid\_IP and the activation function generates a 8-bit output. Figure 6 shows the schematic view of Sigmoid\_IP.

 


Figure 6: Sigmoid\_IP Schematic

## 5. node\_func

Finally, we create a module to contain together the MAC\_ACC and sigmoid\_func modules together. We write a testbench to read the weights and pixels from the file. Then we provide these as input to the node\_func module. As seen in schematic 7, Inside node\_func module, MAC\_ACC module takes pixel, weights, bias, clk and rst as input and outputs a 22 bit weighted sum. This sum is taken by sigmoidFunc as input and the sigmoid activation function gives final output for that particular hidden node.

 


Figure 7: node\_func schematic

On behavioral simulation, post-synthesis functional and post-synthesis timing simulation, we obtain the correct waveform and the final outputs are also correct. The two waveform are shown in figure 8, 9 and 10. The timing report in figure 11 also shows that no timing constraints are violated.



Figure 8: Behavioral Simulation

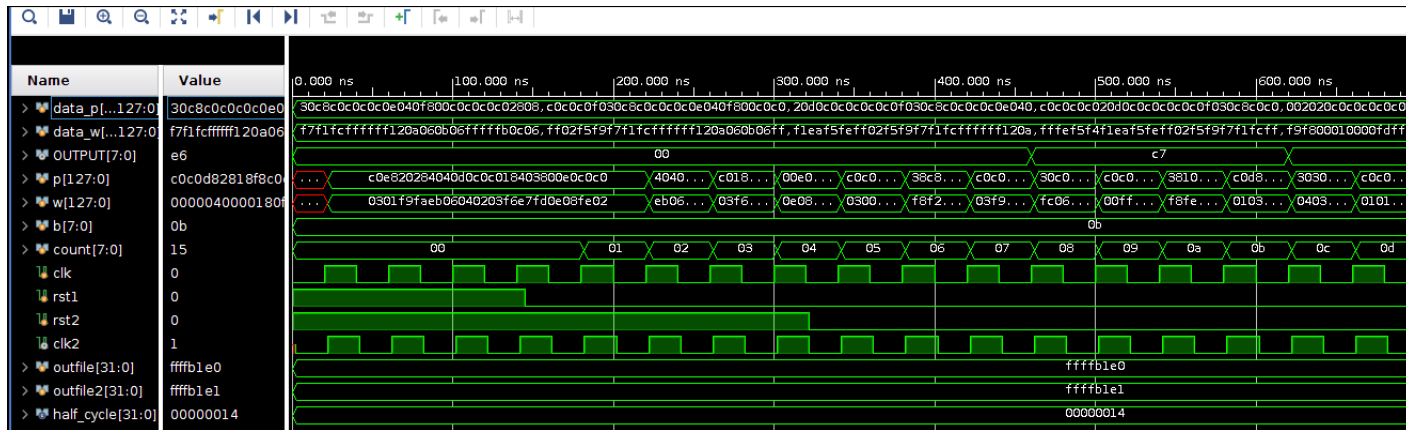


Figure 9: Post Synthesis Functional Simulation

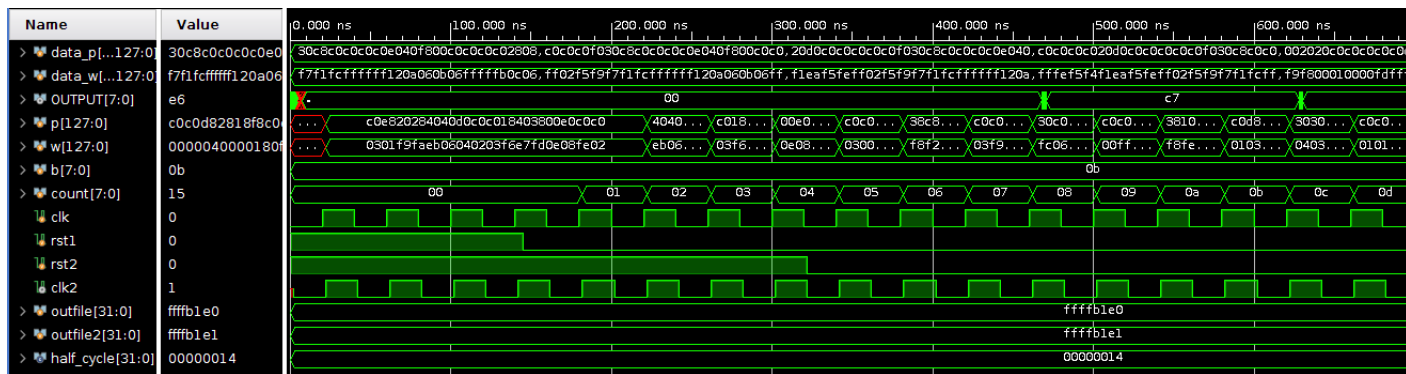


Figure 10: Post Synthesis Timing Simulation

#### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 12.601 ns	Worst Hold Slack (WHS): 0.154 ns	Worst Pulse Width Slack (WPWS): 9.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 216	Total Number of Endpoints: 216	Total Number of Endpoints: 456
All user specified timing constraints are met.		

Figure 11: Timing Report